



LEB 2001

The CMS HCAL Data Concentrator: A Modular, Standards-based Design

A Review of the CMS HCAL DAQ


Gueorgui Antchev, [Eric Hazen](#), Jim Rohlf, Shouxiang Wu
Boston University

Drew Baden, Rob Bard, Rich Baum, Hans Breden,
John Giganti, Tullio Grassi, Aaron McQueen, Jack Touart
University of Maryland

Mark Adams, Kyle Burchesky, Weiming Qian
University of Illinois, Chicago

Wade Fisher, Jeremy Mans, Chris Tully
Princeton University

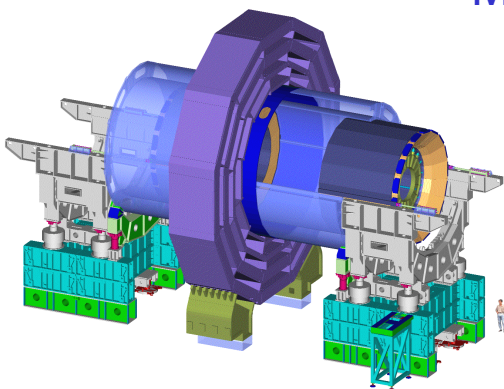J. Elias, T. Shaw, J. Whitmore...
Fermi National Laboratory





Outline



LEB 2001

- HCAL Trigger DAQ Overview
 - Requirements
 - Overview Diagram
 - DAQ Crate
- HCAL Trigger Readout Card (HRC)
 - Requirements
 - Block Diagram
 - Photo
- HCAL Data Concentrator (DCC)
 - Motherboard
 - Link Receiver
 - Logic Board
- HCAL Readout Controller (HRC)
- Data Format
- System Tests
- Summary



HCAL Trigger/DAQ Requirements



LEB 2001

- Digitize scintillator pulses every BX
 - Pulses occupy ~3 BX periods (25ns each)
 - Dynamic range required is about 10^4 (14-15 bits)
 - QIE (custom floating point ADC) used
- Reliably assign energy measurement to a single BX for Level 1
 - F.I.R. filter implemented in FPGA (ala FERMI)
 - Synchronized across HCAL+ECAL for input to Level 1
- Transmit data to DAQ on L1A
 - Zero Supression
 - Formatting




HCAL FE/DAQ Overview



LEB 2001

Readout Box (RBX)
(On detector)

DAQ Crate
(in UXA)

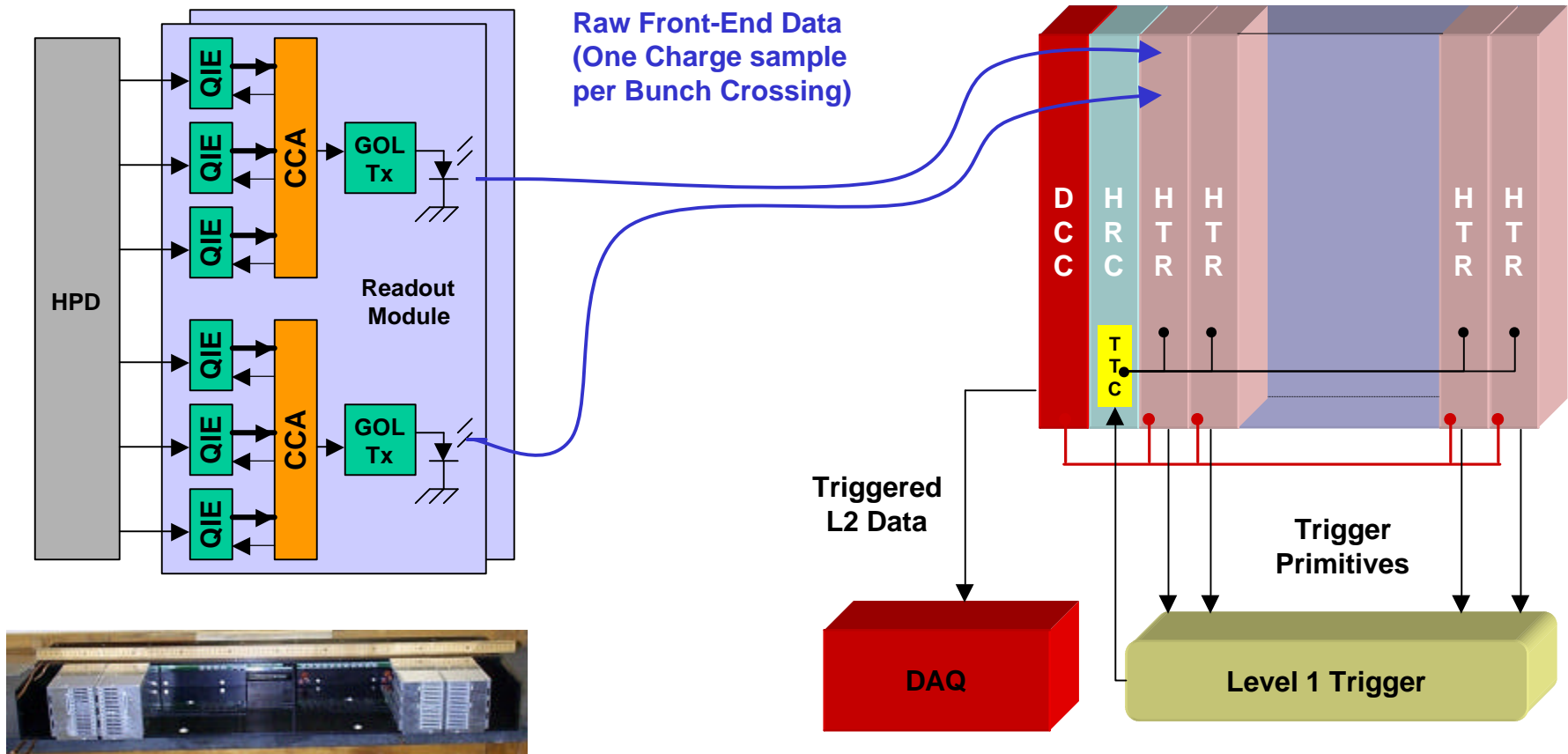



HCAL Channel Counts



LEB 2001

Region	Towers	GOL Fibers	Trigger Towers	Crates
Barrel	2,160	720	2,160	6
Outer	2,160	720	0	6
Endcap	2,160	720	1,728	2
Forward	2,016	672	144	6
Overlap	864	288	144	6
Total	9,360	3,120	4,176	26




HCAL DAQ Crate



LEB 2001

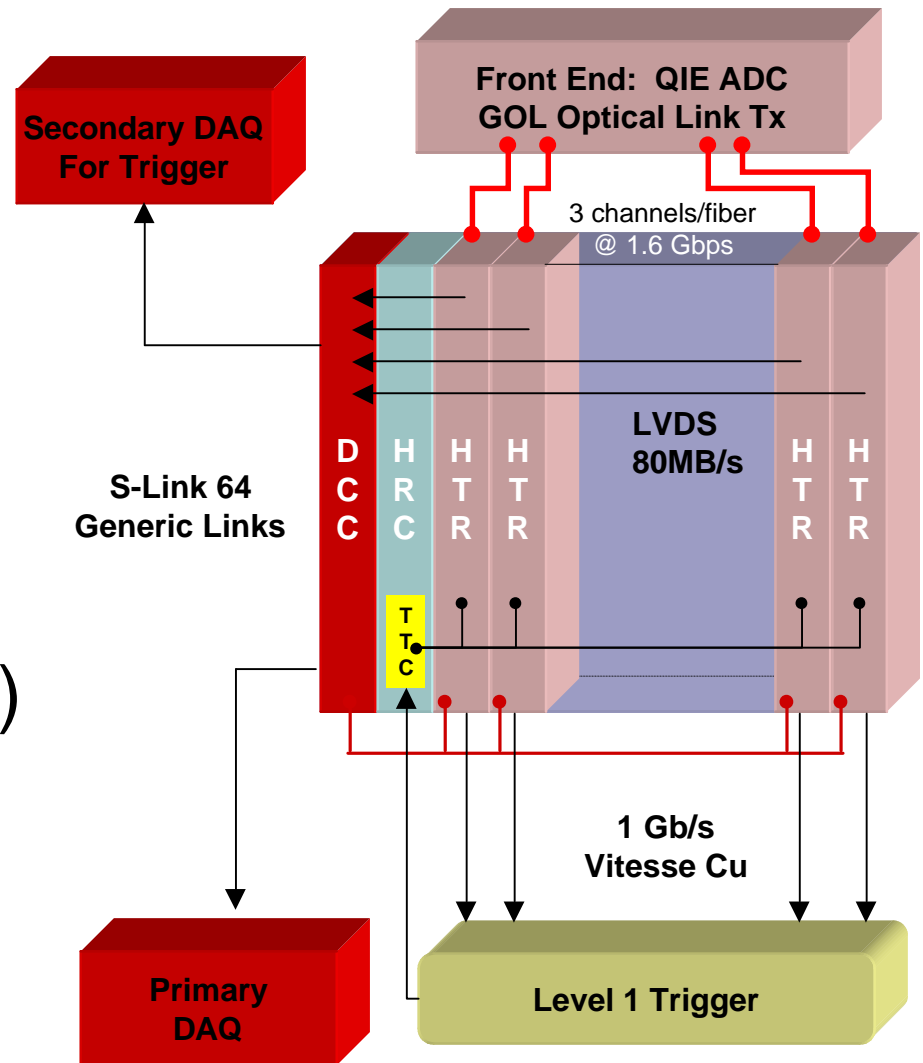- 9U x 400 VME64x Crate
- Controller (HRC)
 - Commercial CPU/Bridge
 - TTC Fanout
- Readout Cards (HTR)
 - Front-end data in (GOL)
 - Level 1 Out (Vitesse Cu)
 - Level 2 Out (LVDS)
- Data Concentrator (DCC)
 - Level 2 in (LVDS) x 18
 - S-Link Out x 2





HCAL Trigger Readout Card (HTR)



LEB 2001


- **Level 1 (Trigger) Path**
 - Energy Sum and Bunch Crossing Determination
 - Output Trigger Primitives to Level 1 synch'd to BX
- **Level 2 (DAQ) Path**
 - Zero-suppress Level 2 data (energy filter)
 - Package raw data plus trigger primitives
 - Send to Data Concentrator every L1A
- **Implementation**
 - FIR filter for bunch crossing (ala FERMI)
 - Single large FPGA for core logic



HCAL Trigger Readout Card



LEB 2001

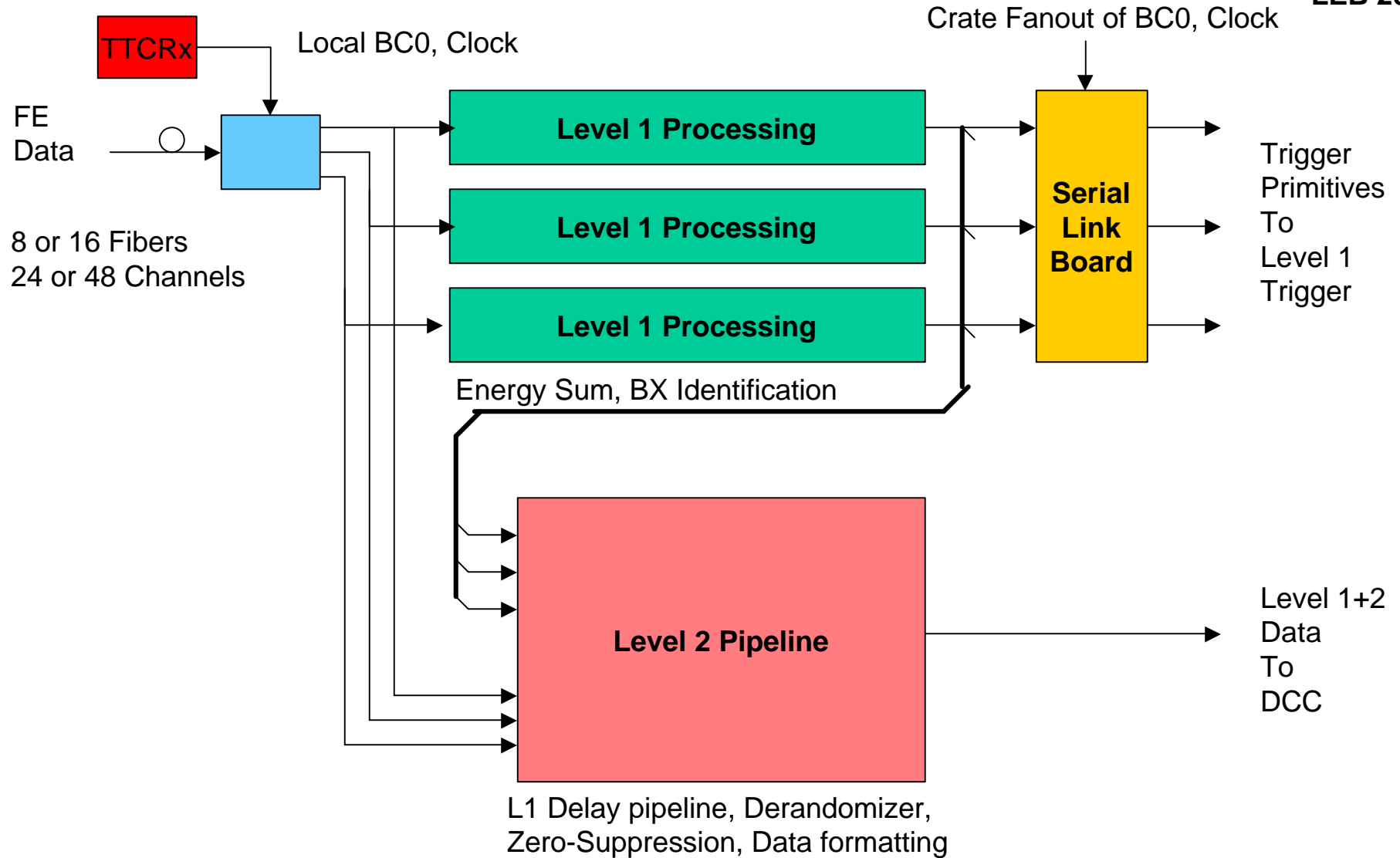




HCAL Trigger Readout Card



LEB 2001

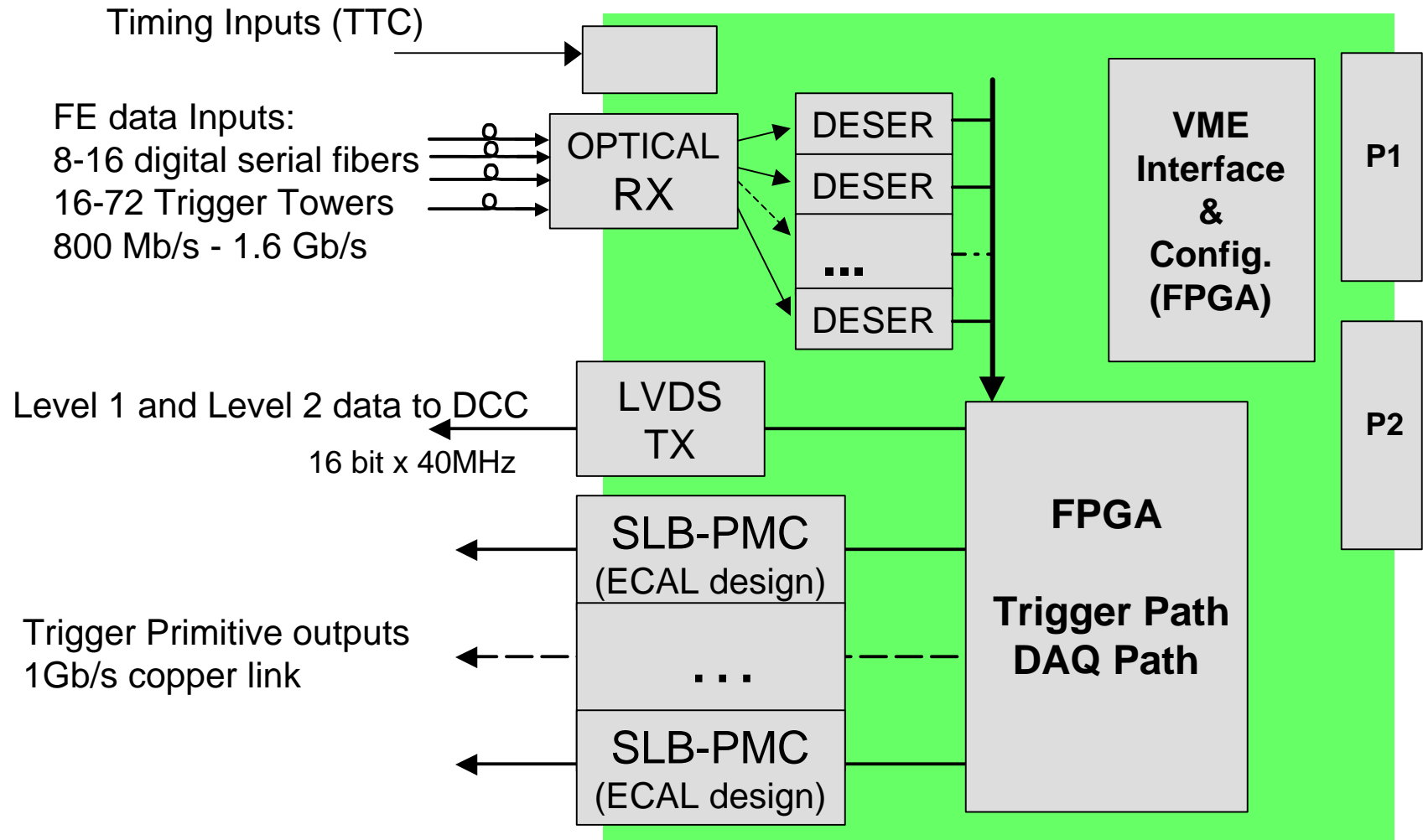




HTR Demonstrator Board



LEB 2001

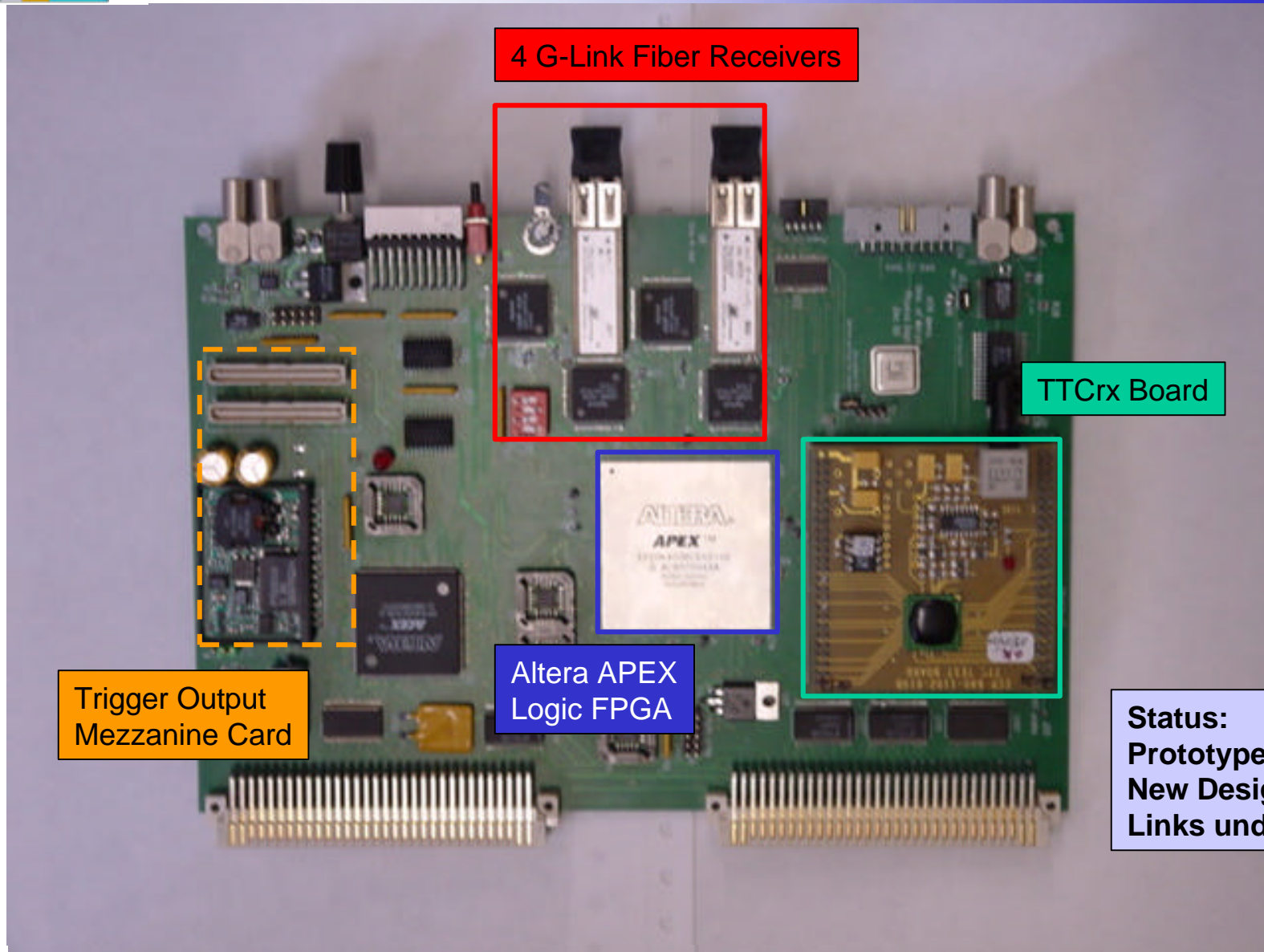




HCAL Data Concentrator



LEB 2001

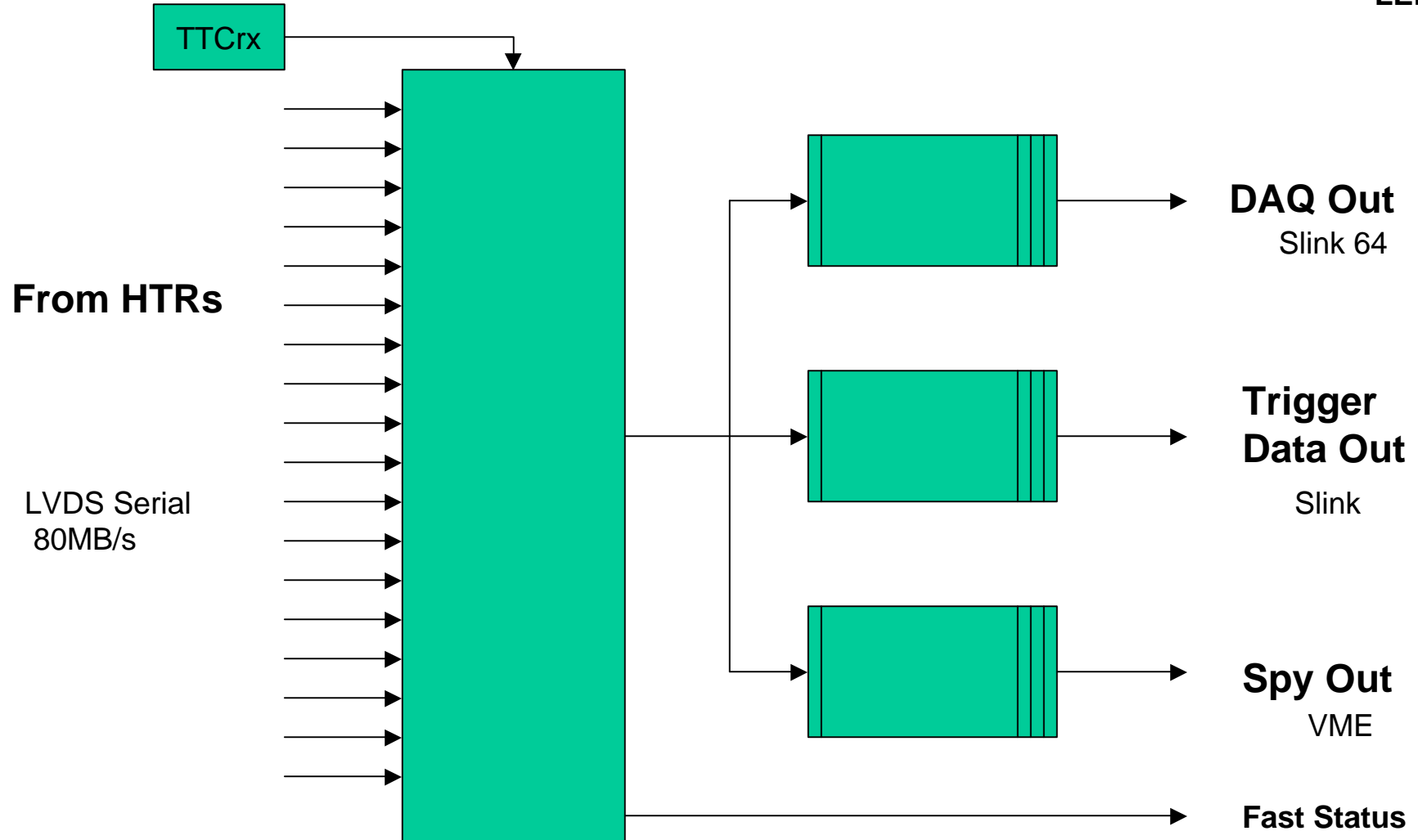




HCAL DCC Prototype Architecture



LEB 2001

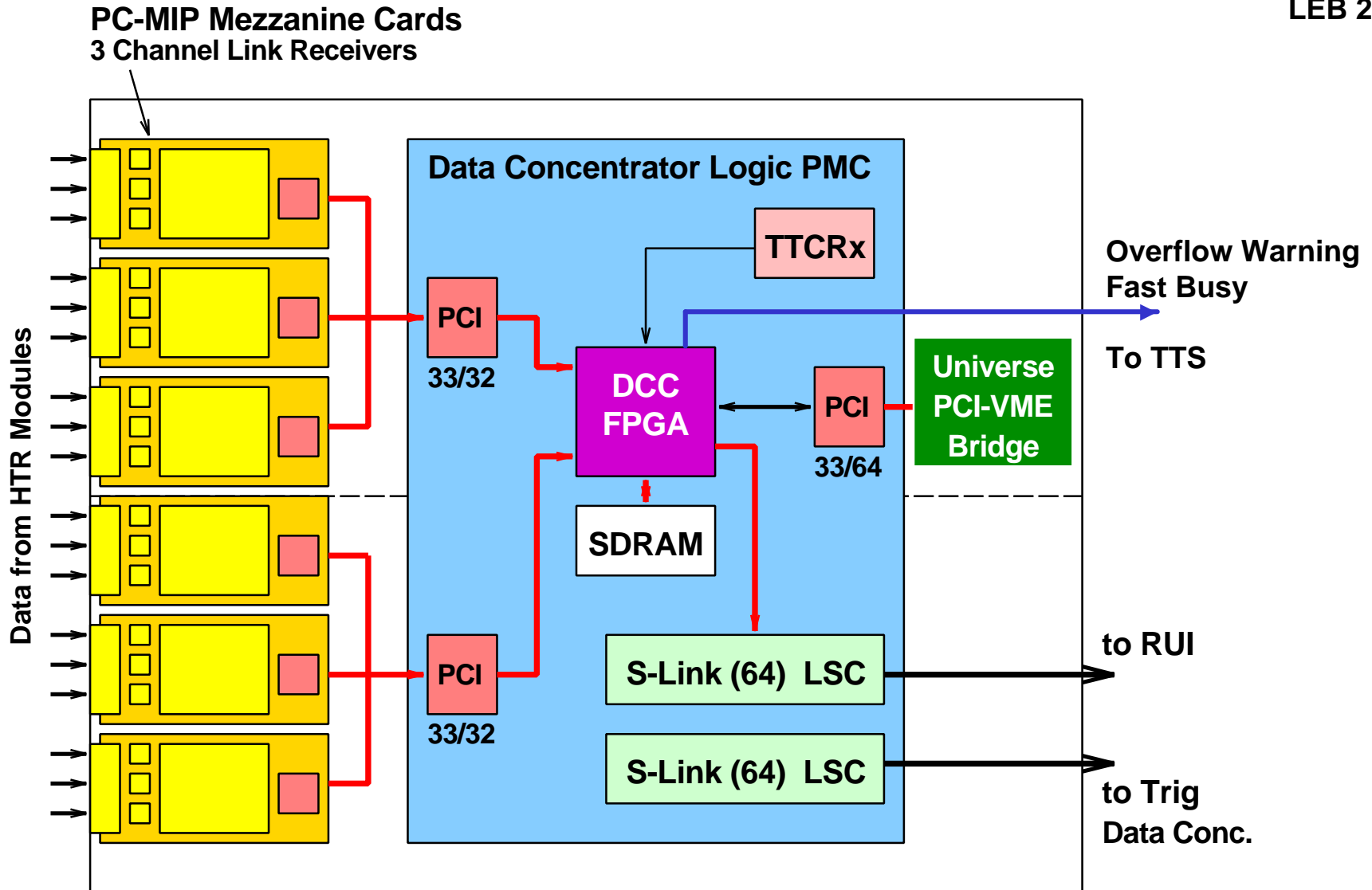




HCAL DCC Motherboard



LEB 2001

3-Channel
LVDS
Receivers

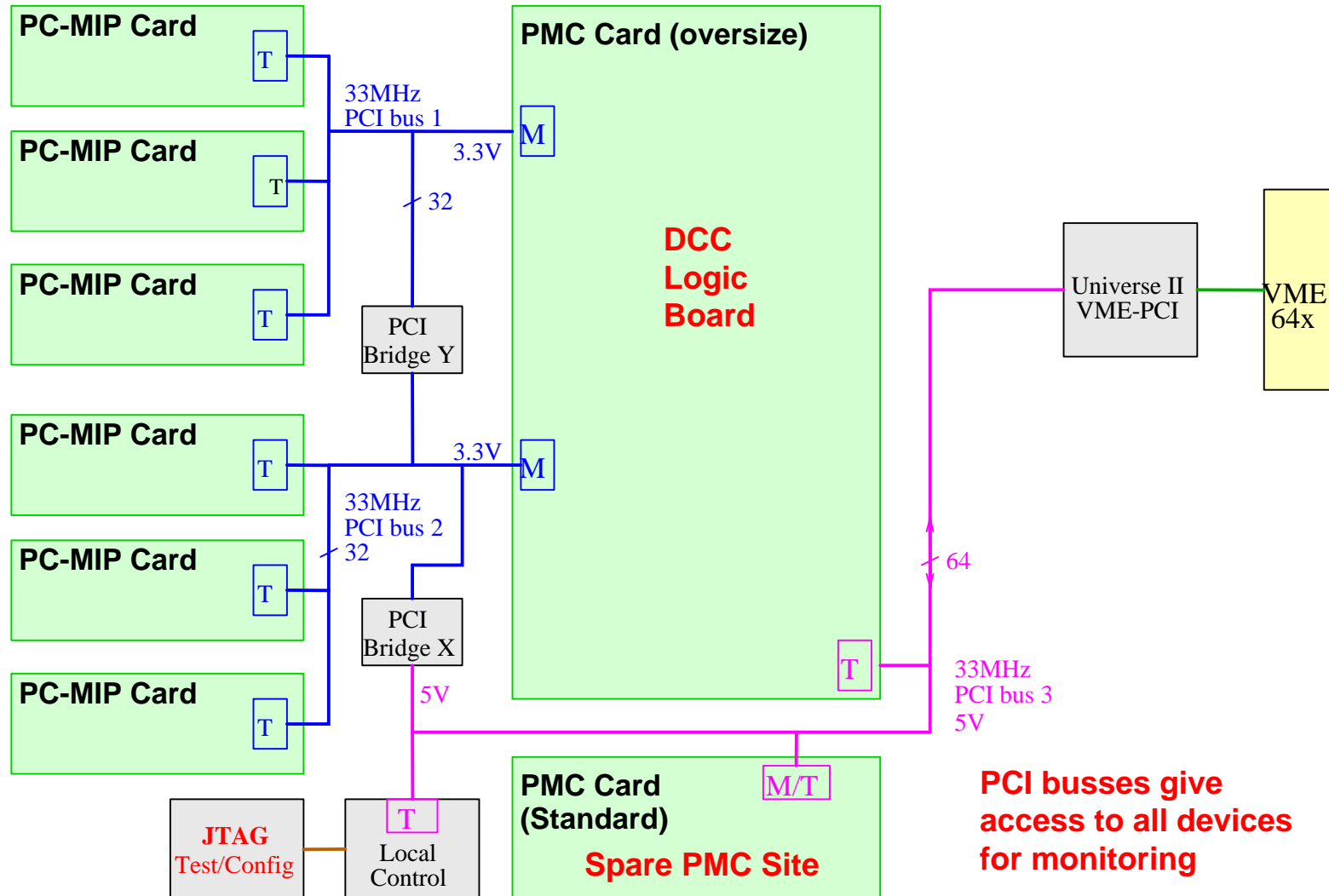




HCAL DCC Motherboard



LEB 2001

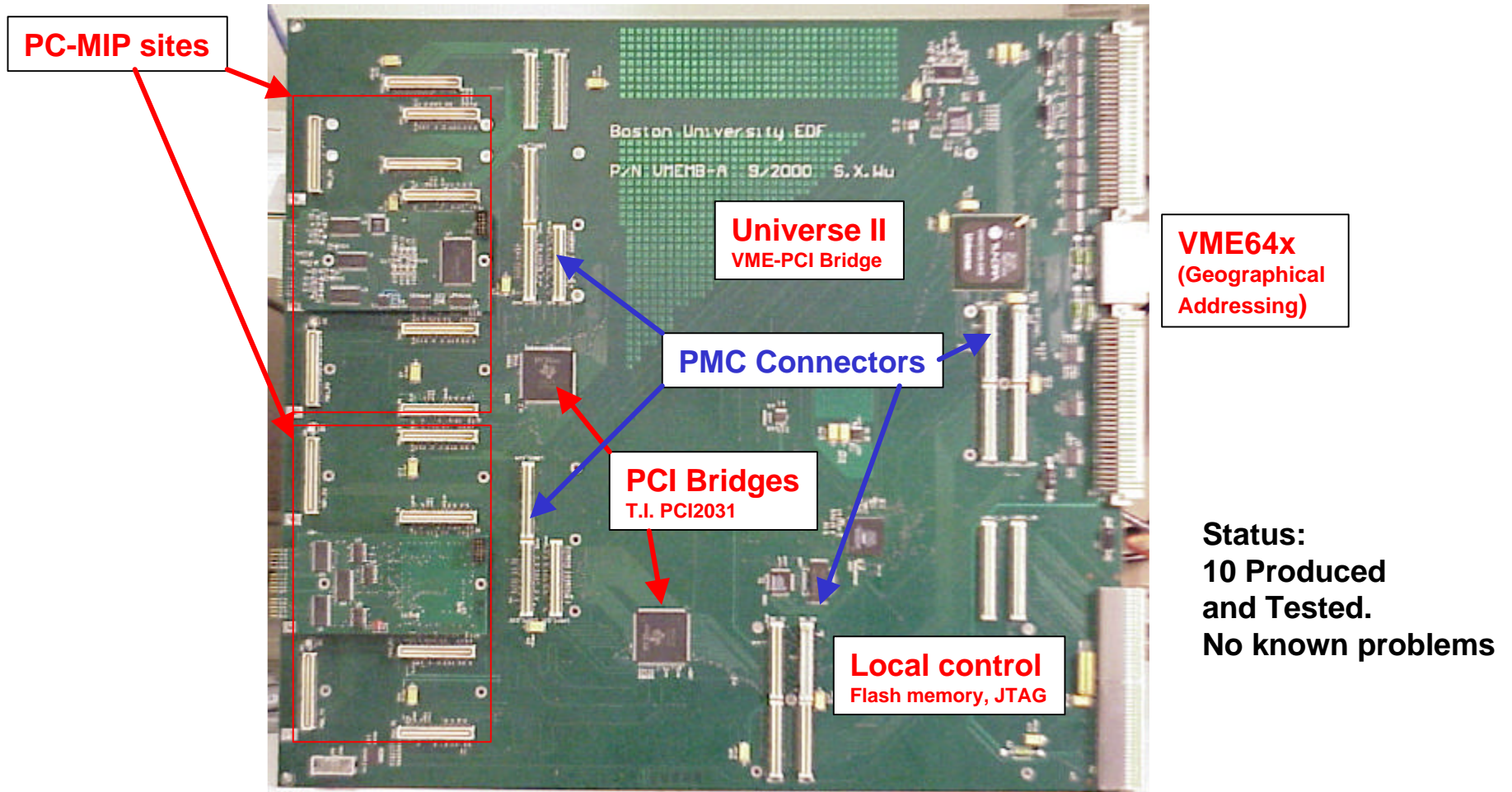





PC-MIP 3 Channel Link Receiver



LEB 2001

- 3 “Channel Link” LVDS receivers
- PCI target interface
- On-board logic:
 - ECC (Hamming) plus parity
 - Correct 1-bit, detect multi-bit errors
 - On-the-fly Event Building
 - Event number checking
 - Overflow warning (discard data payload on overflow)
 - Missing header/trailer detection & repair
 - Monitoring:
 - Count of words, events, errors
 - Status update on “marked” event for synchronization of monitoring
 - Status: 20 second-generation prototypes build (design is done)

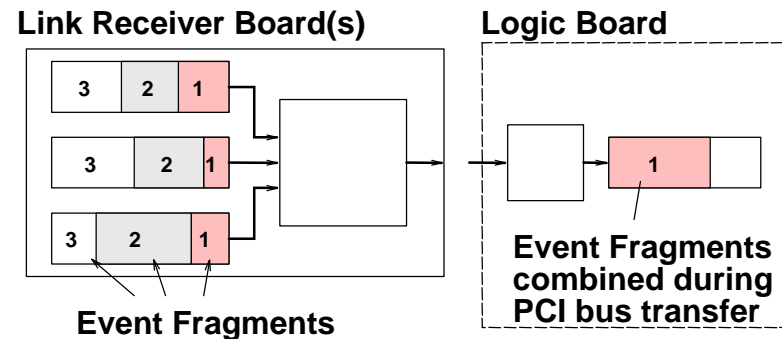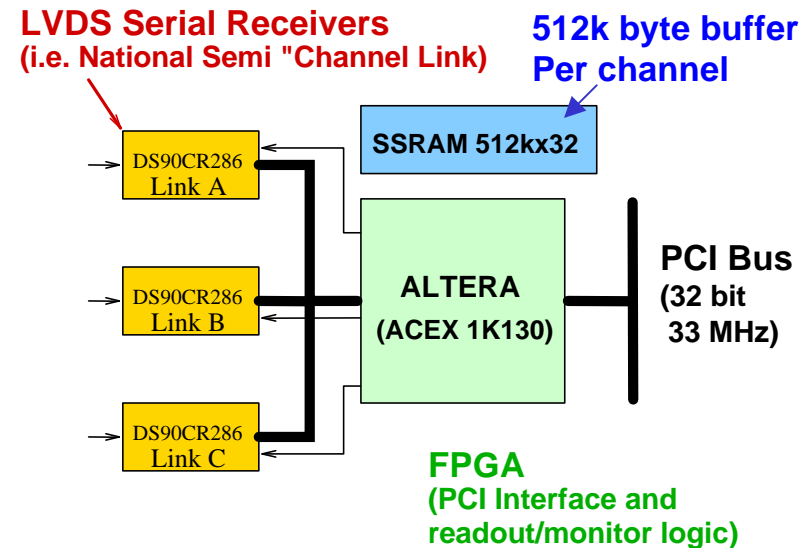




PC-MIP 3-Channel Link Receiver



LEB 2001

Altera ACEX FPGA
EP1K100FC484-1

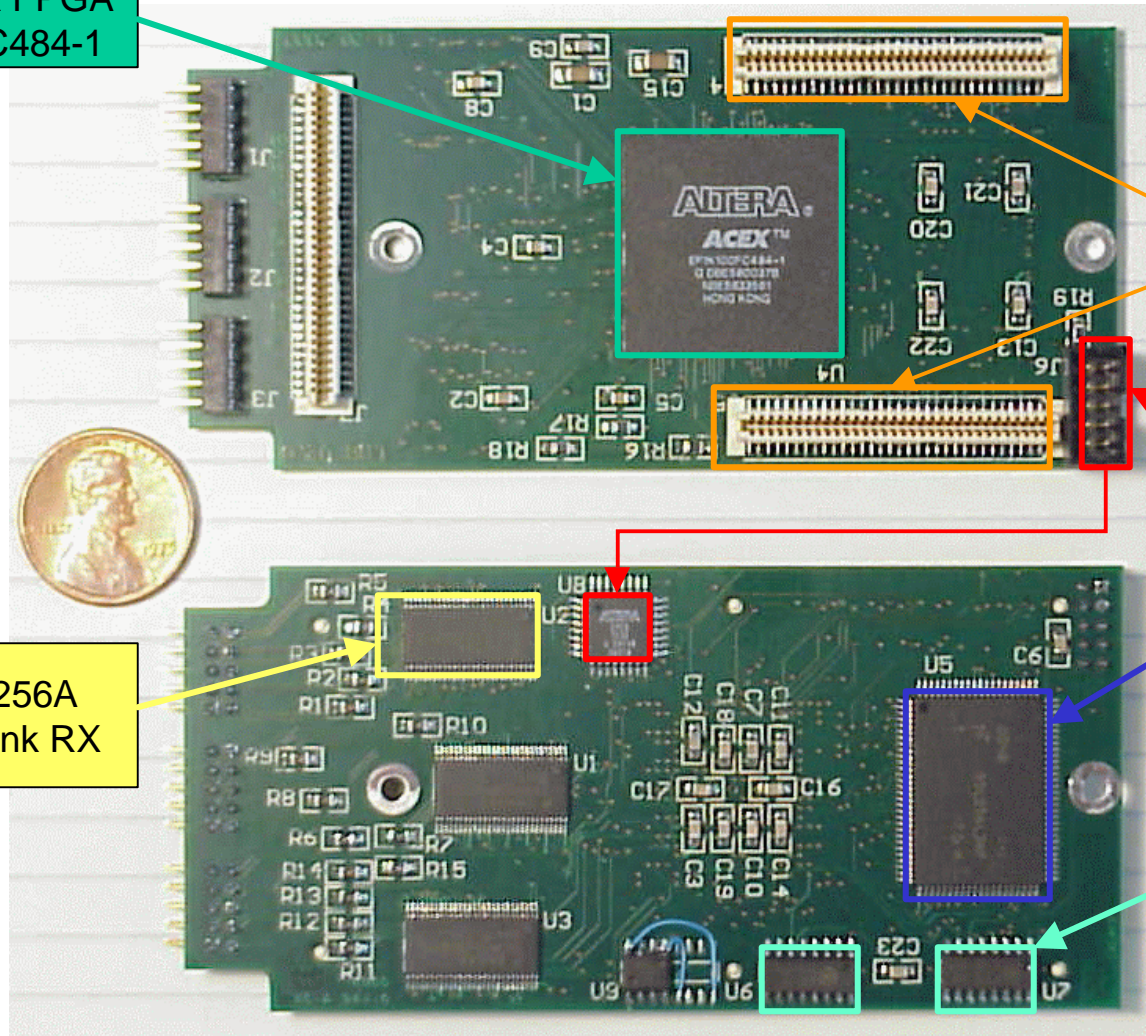

PC-MIP Interface
(PMC 33MHz 32 bit)

Programming Connector
For flash memory

DS90CR256A
Channel-Link RX

MT55L512V ZBT
512Kx32 SSRAM


Cypress Clock
Multipliers



DCC Logic Board



LEB 2001

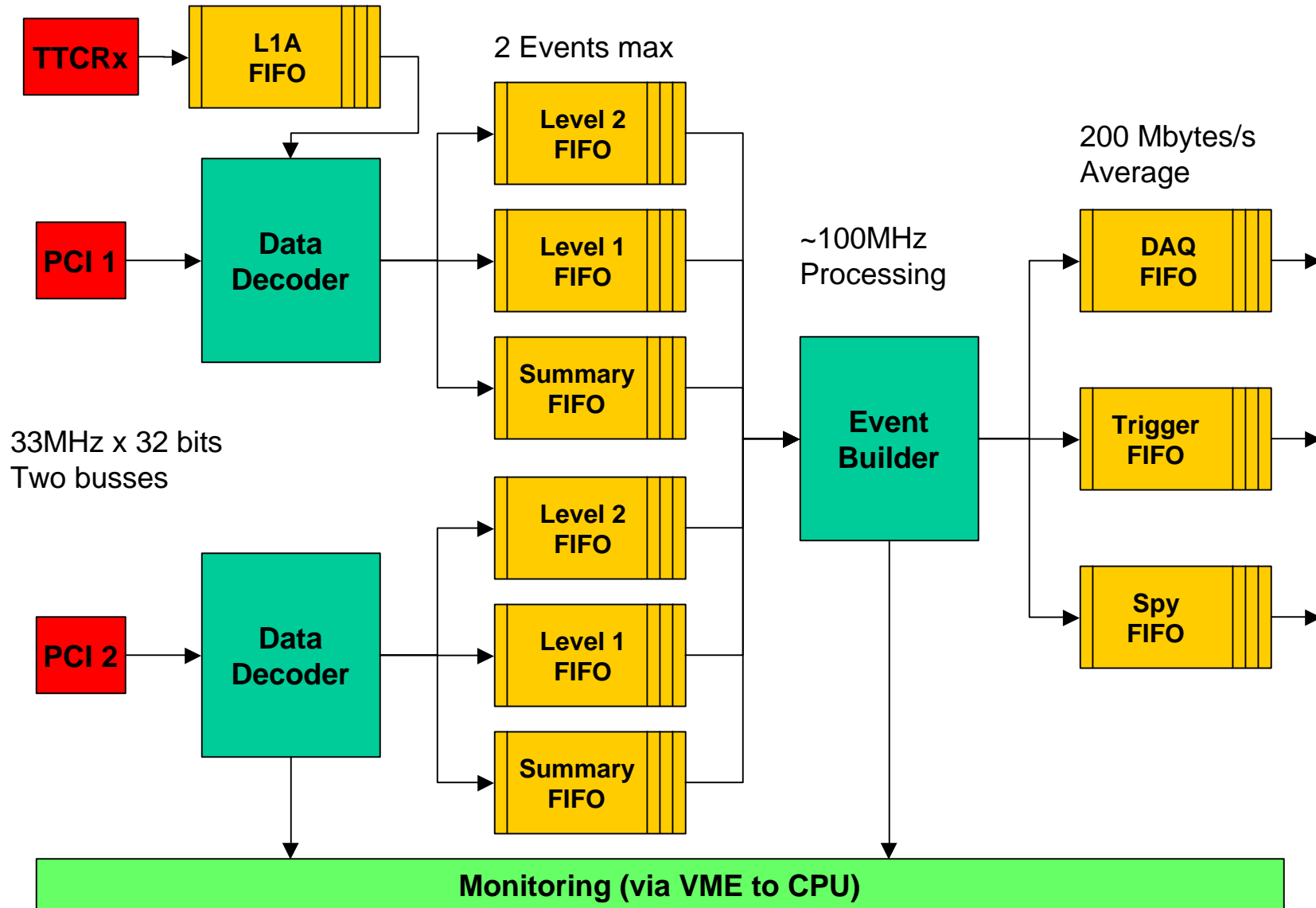



DCC Prototype Logic Board




LEB 2001

- Features:

- On-board TTCrx controls operation
- 3 Altera FPGAs for PCI interfaces (use Altera PCI-MT/32 core)
- Xilinx Virtex-2 contains all other logic:
 - Event Builder
 - Monitoring
 - Buffering (DDR SDRAM interface at 800Mbytes/s)
 - S-Link output (32 in demo; 64 final)
- On-board flash memory for FPGA initialization
- JTAG Interface

- Status:

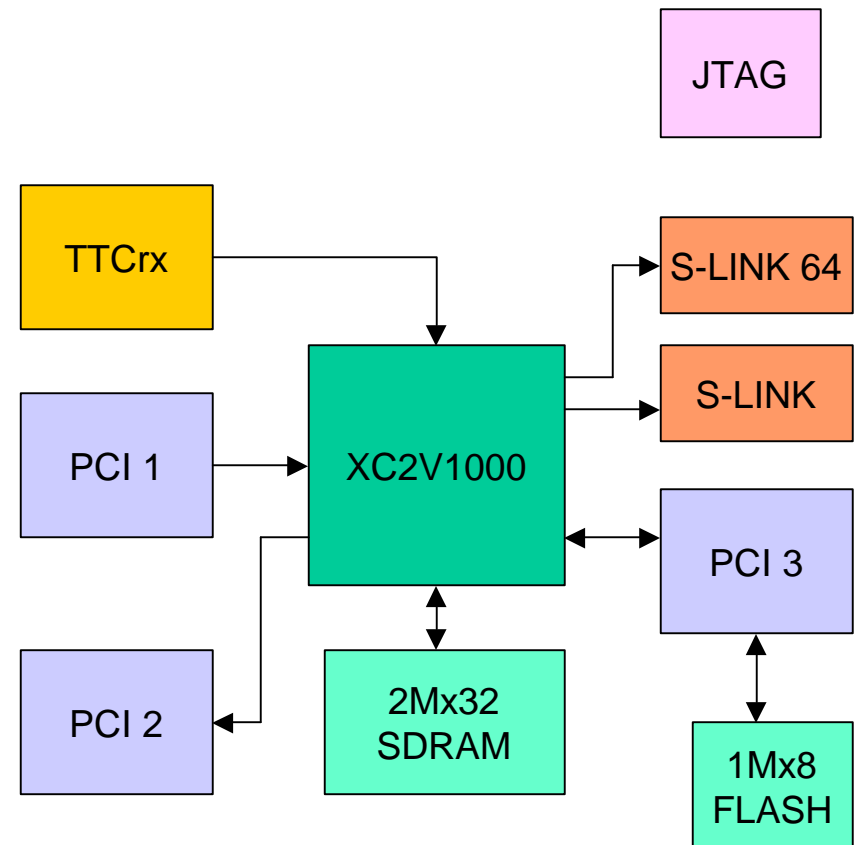- Prototype PCB Working
 - Continuous DAQ transfer at 80MB/s demonstrated (one PCI bus only)
- 2nd Prototype layout done



DCC Prototype Logic Board

PCI-3
64 bit
33 MHz

DDR SDRAM

Xilinx
XC2V1000


TTCRx
PCB (back)

PCI-1
32 bit
33 MHz


HTR inputs
1-9

PCI-2
32 bit
33 MHz

HTR inputs
1-9

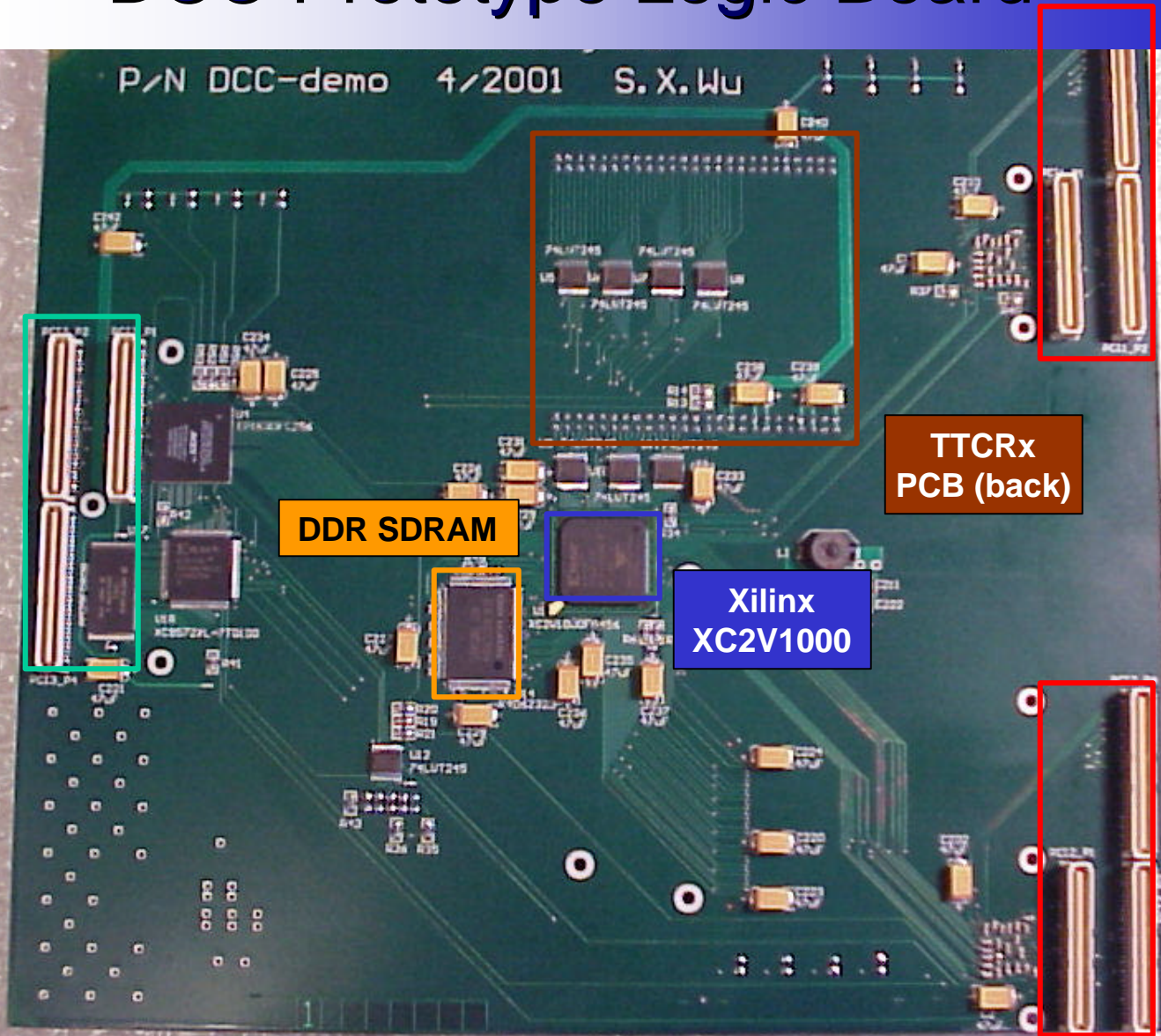

DCC Prototype Logic Board

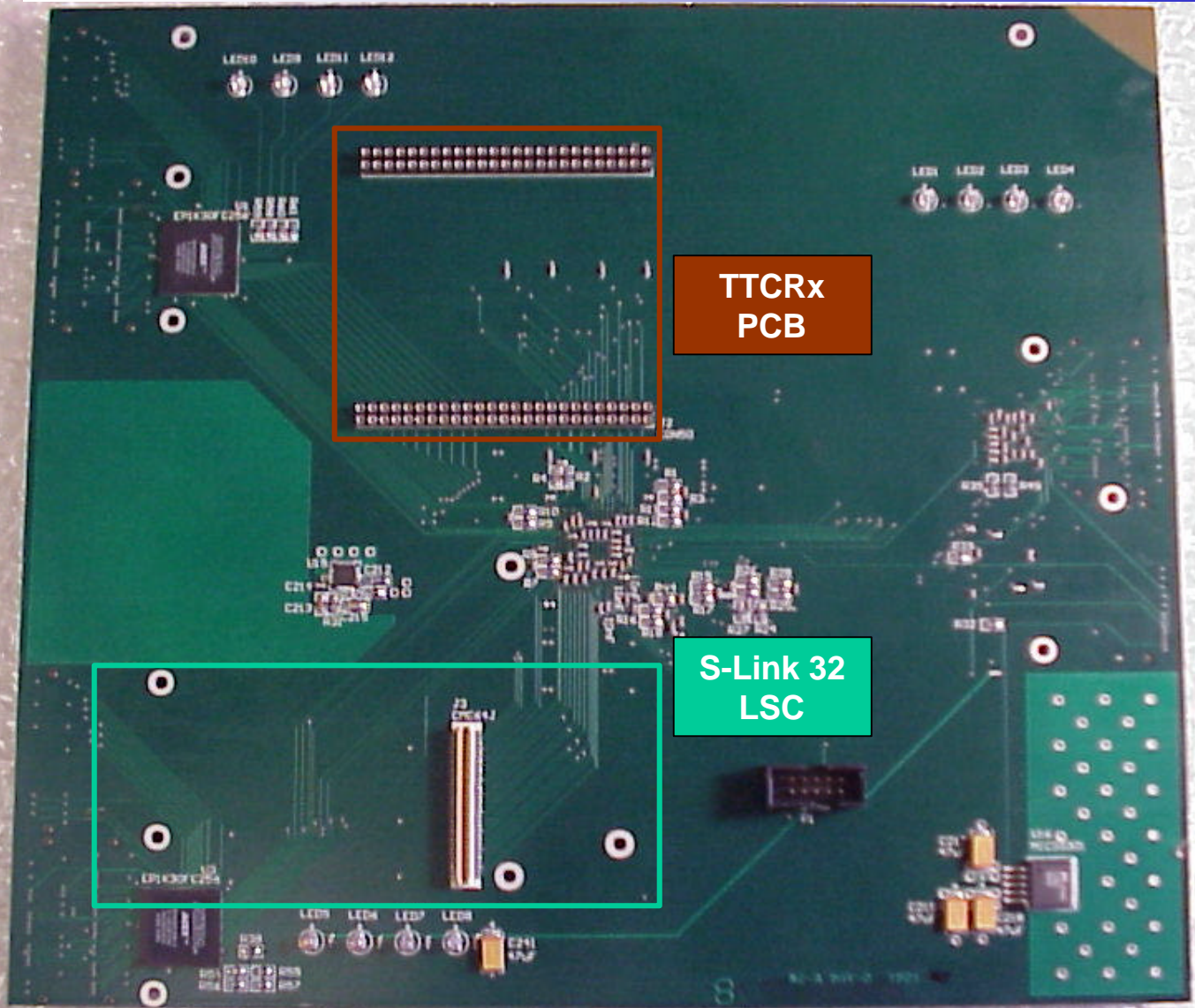

TTCRx
PCB


S-Link 32
LSC



Data Concentrator Demonstrator



LEB 2001

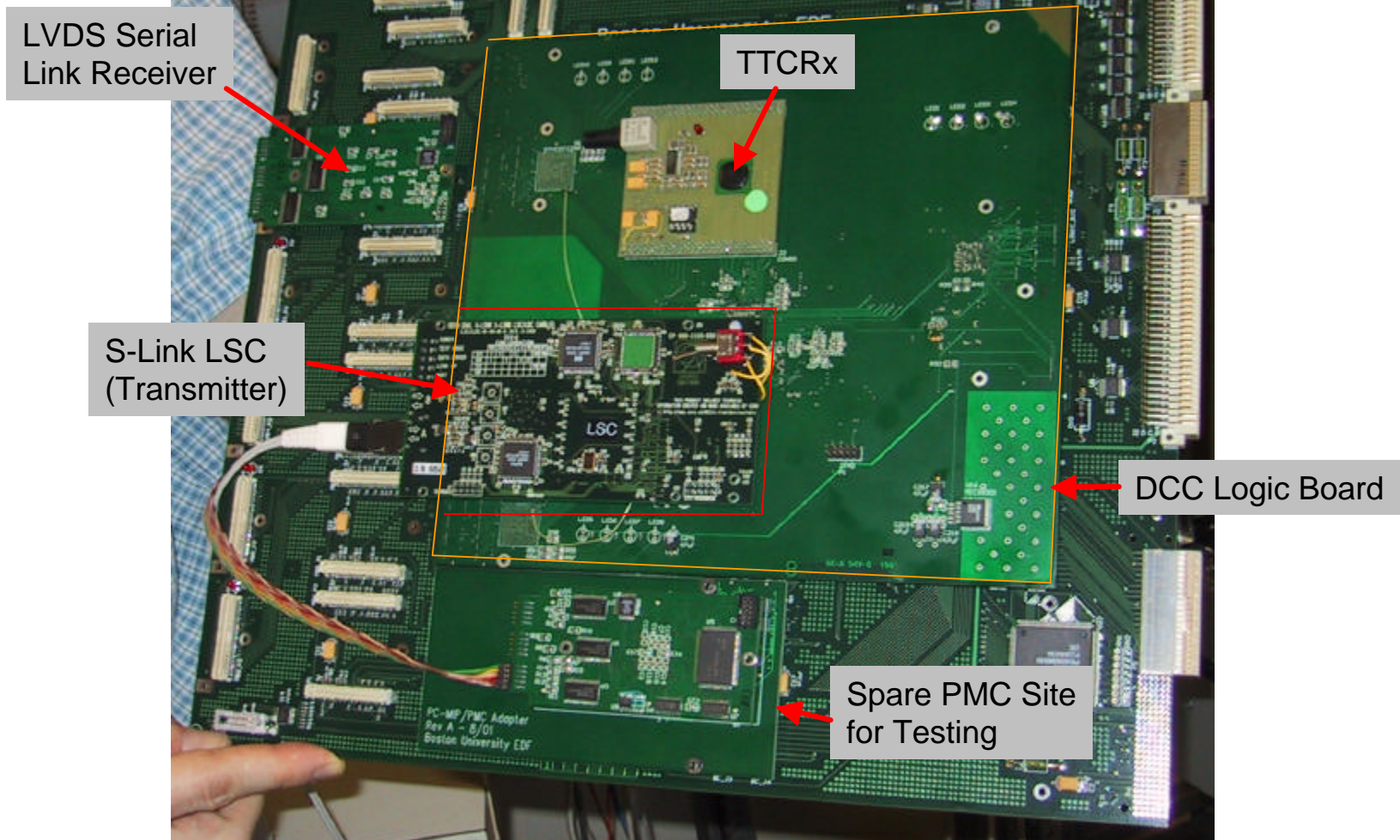




HCAL Readout Controller (HRC)



LEB 2001

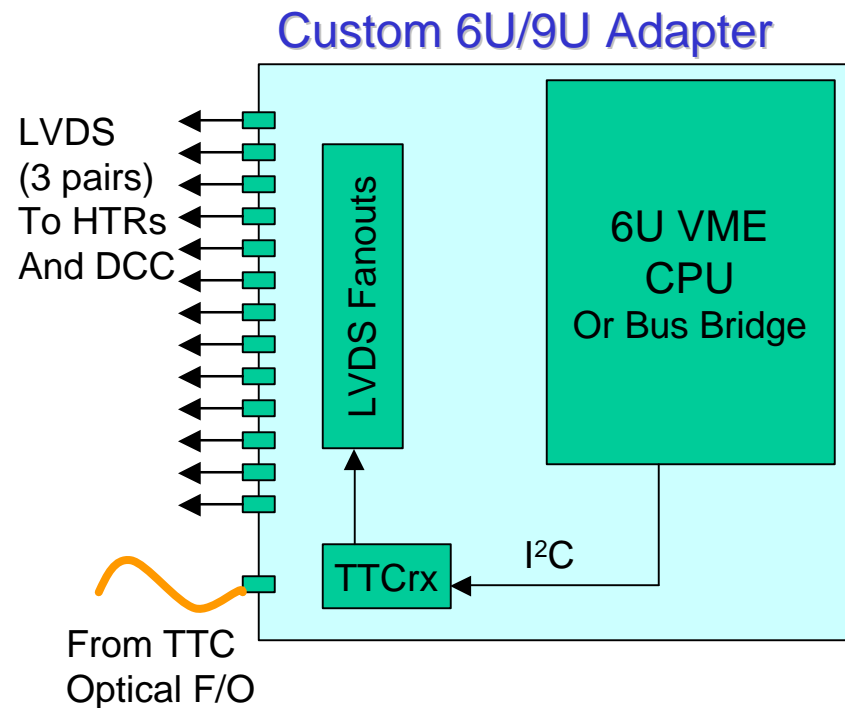- Run Control
 - Initialization, shutdown
 - “Slow” monitoring via VME
 - Error recovery:
 - Monitor status registers of modules via VME
 - Report serious errors via DCS
 - Reset/Restart on command
- TTC Fanout
 - Fanout encoded TTC to all modules
 - Fanout Locally Decoded CLK, BC0 to HTR modules
 - I²C Control of local TTCrx






HCAL DAQ Data Format



LEB 2001

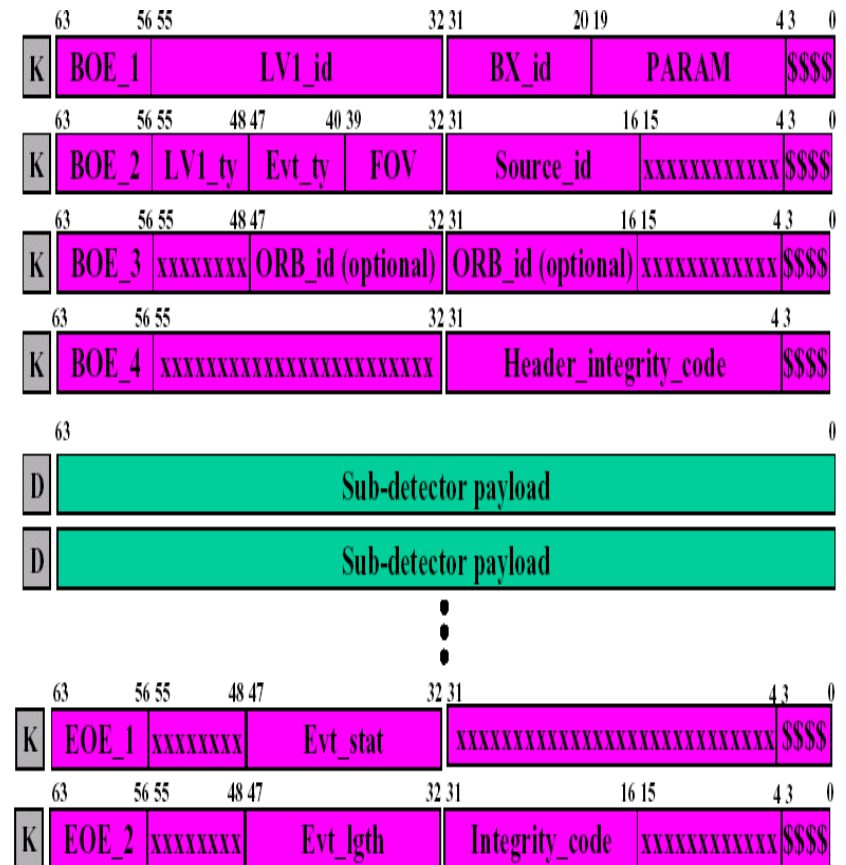- Data format follows TriDAS Guidelines → → →
- HCAL payload: (details t.b.d)
 - Raw QIE (ADC) samples
 - Level 2 Filter output
 - Trigger Primitives
 - Zero-suppression mask
 - Error summary:
 - Front-end errors
 - Uncorrected Link errors
 - Synchronization errors
- We will stay tuned for updates to the data format → → →





System Tests



LEB 2001

- **Radioactive Source Calibration Test**
 - NOW at Fermilab
 - Record data at 80Mbyte/s for detector calibration
 - Uses demonstrator hardware for all system components and verifies basic functionality
- **Test Beam – Summer '02 at CERN**
 - Record data at realistic LHC rates
 - A few hundred channels
 - Uses (2nd) prototype hardware for all components
 - Verify high-rate operation under realistic conditions



Summary




LEB 2001

- **Front-End:**
 - RBX Mechanics/Cooling Designed+Prototyped
 - Readout Card prototypes under test
- **HTR:**
 - 6U Demonstrator prototypes working
 - New prototype with GOL under design
- **DCC:**
 - 9U Demonstrator prototypes working
 - No major changes anticipated for production version (significant FPGA coding remains)
- **HRC:**
 - Use commercial CPU for now
 - TTC Fanout Design Done (U.I.C.)
- **Major Concerns:**
 - QIE Performance (pending prototype tests now underway)
 - Performance of 1.6 Gbit GOL link
 - HTR/DCC FPGA Design – Quite complex

HCAL RBX



HTR Demonstrator

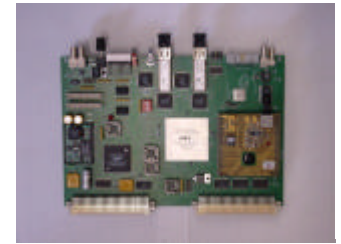

DCC Demonstrator



VME Pentium CPU





LEB 2001


Backup Slides



HCAL DAQ Buffering



LEB 2001

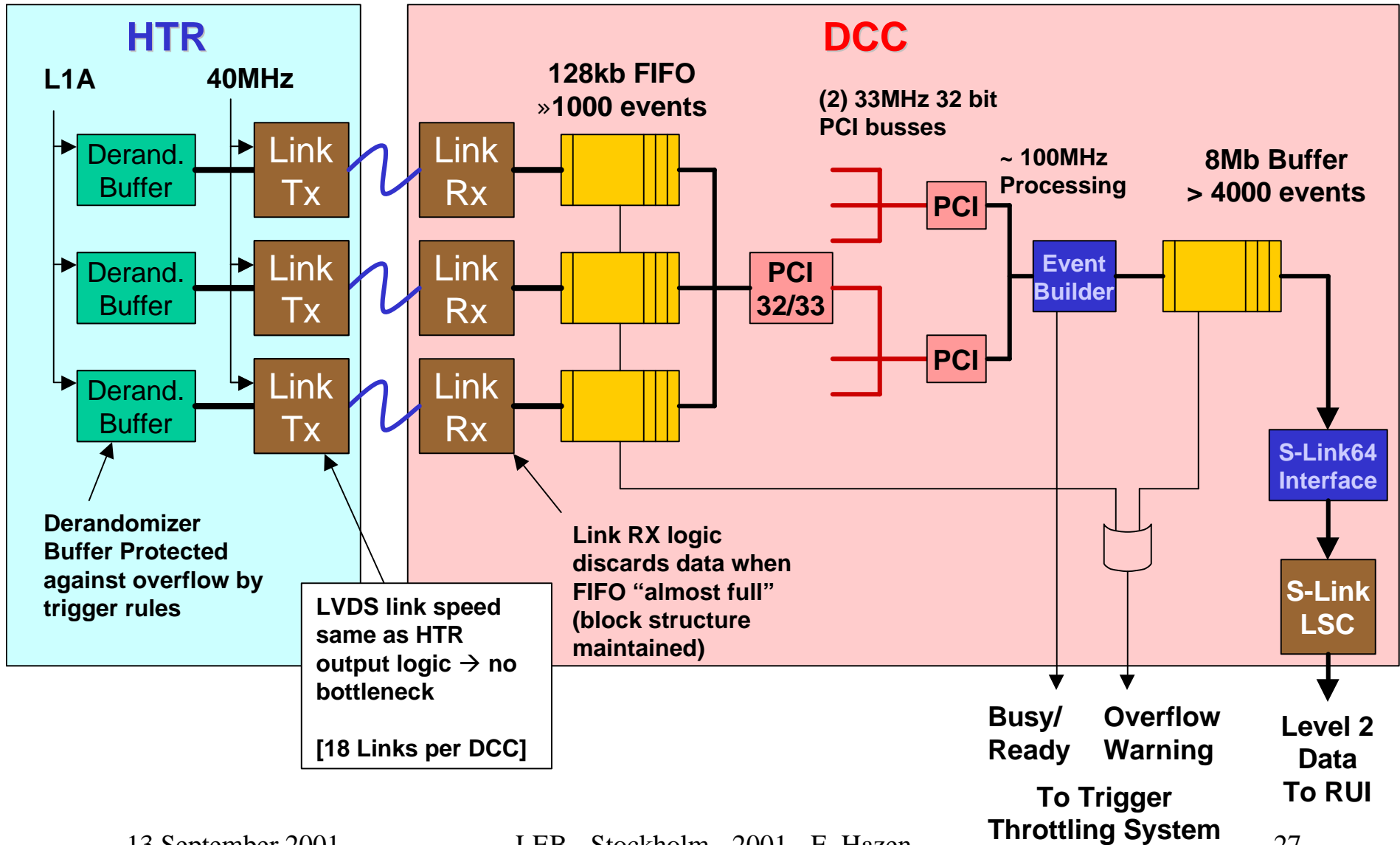




HCAL Timing / L1A Distribution




LEB 2001

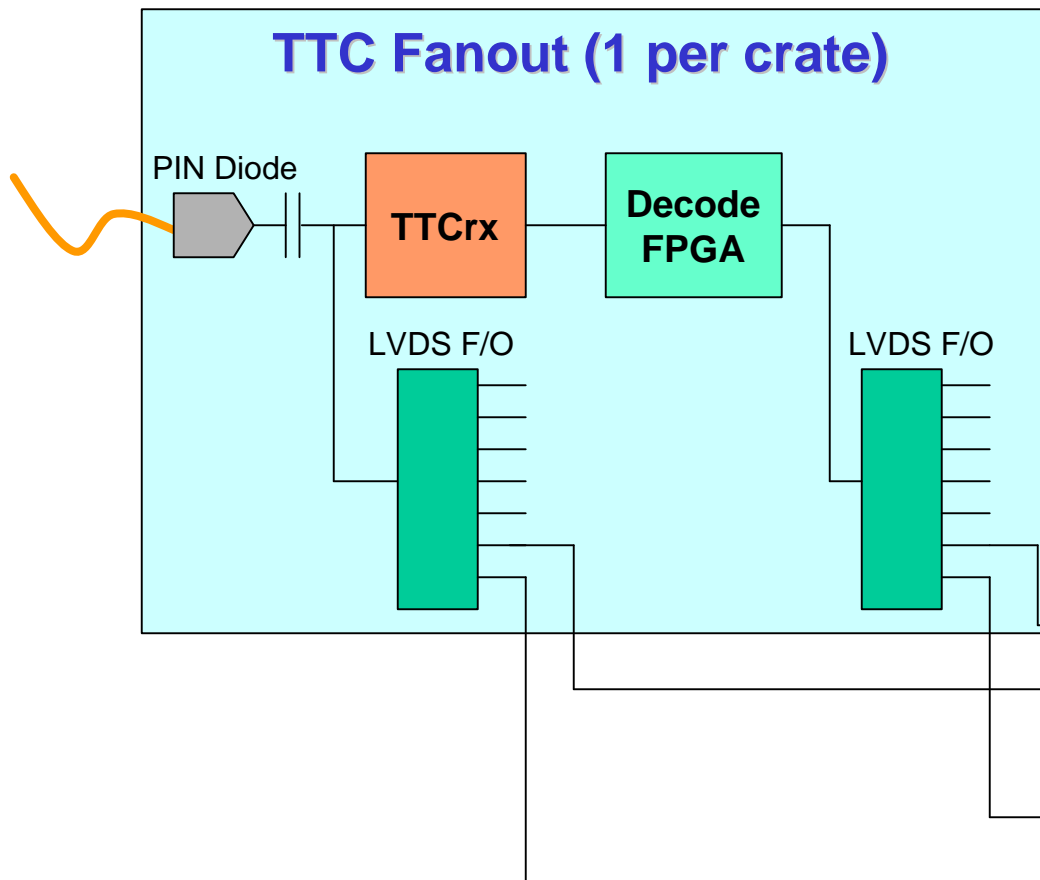

Fanout Both:

- Encoded TTC signal
 - For synchronization with incoming FE data (individual skew control)
- Decoded BC0, CLK
 - For synchronization across all HCAL and ECAL of TPG to Level 1
- Similar to ECAL solution (J. Carlos Dasilva)

HTR Cards

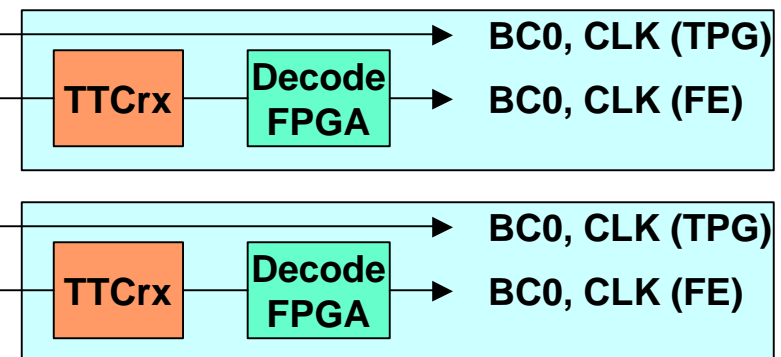



HCAL Controls and Monitoring



LEB 2001


- Fast Controls (via TTC):
 - L1A, Start Run, Stop Run
 - Reset (complete and partial – need to define!)
- Fast Monitoring (dedicated signals to TTS)
 - Overflow Warning (buffer full above preset limit)
 - Busy/Ready (reset, start/stop completed)
- Slow Monitoring (link errors, loss of sync, etc)
 - Counters in FPGAs collect information in real time
 - Reported via CPU



HTR Details



LEB 2001

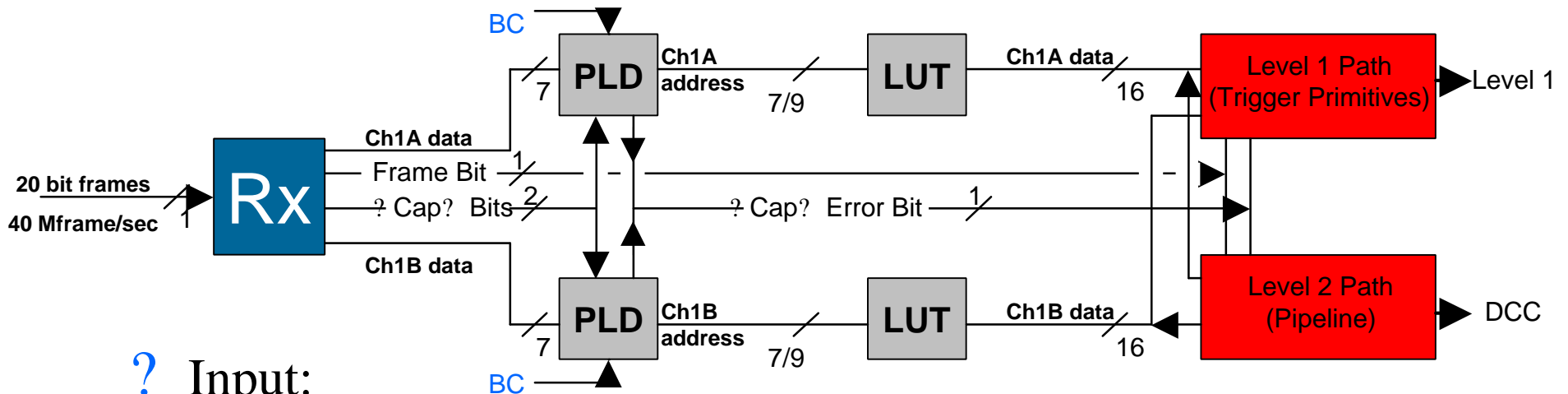

? Input:

? QIE 7 bit floating plus 2 bits ? cap?

? Lookup table (LUT)

? Convert to 16 bit linear energy

? Pipeline (? Level 1 Path?)

? Transmit to Level 1 trigger, buffer for Level 1 Accept, 3 μ s latency

? Level 2 Buffer (? Level 2 Path?)

? Asynchronous buffer, sized based on physics requirements




PCI Development



LEB 2001

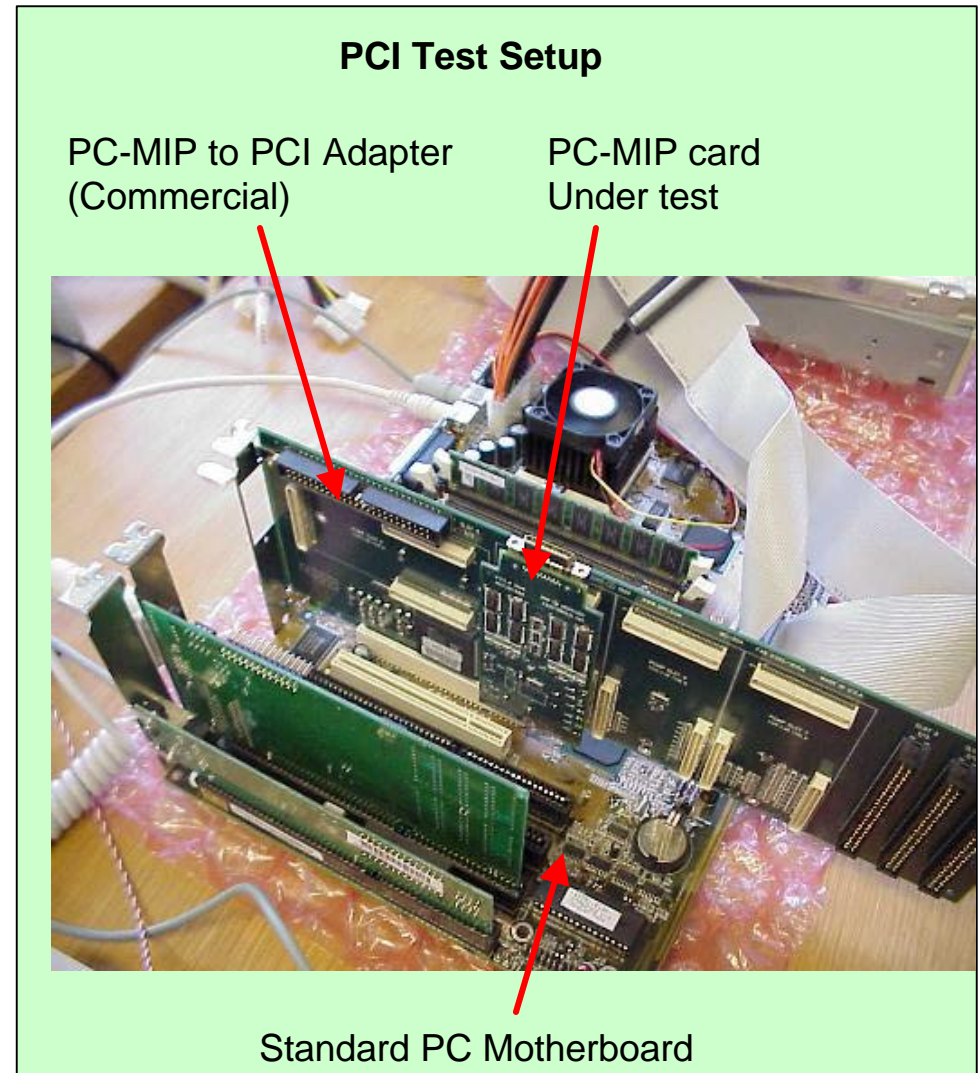- PC-MIP Cards
 - Use adapter in standard PC motherboard
 - LRB Prototype was completely developed before motherboard
- VME Motherboard
 - Test all sites with standard PC-MIP and PMC cards
- Integration
 - Integration of motherboard and mezzanine cards was quite smooth
- PCI Interface logic
 - Use Altera Core (motherboard and logic boards)
 - Own design simple slave for LRB





Flash ADC Quantization



LEB 2001

Bins: $16 \cdot 1 + 7 \cdot 2 + 4 \cdot 3 + 3 \cdot 4 + 2 \cdot 5$ (total of 64 units = 480 mV, 1 unit = 0.3 GeV)

Ranges: *1, *5, *5, *5; Pedestal is in bin "3".

Calibration uses additional subset of comparators *3.

